

 
 


 Question Bank of Unit 5: Processor Logic Design

- 1 Define: Microoperation
- 2 Define: Accumulator.
- 3 Define: Status Register.
- 4 List of the micro operations perform by an accumulator.
- 5 Briefly explain the accumulator register in ALU.
- 6 Draw and explain basic block diagram of Processor unit in detail.
- 7 Discuss the effect of output carry in the arithmetic circuit.
- 8 Draw block diagram of ALU and explain ALU in detail.
- 9 Explain how the value of overflow bit is calculated in status register.
- 10 What is micro-operation? Enlist the micro-operation performed by accumulator.
- 11 What is the basic building block of ALU? Design arithmetical unit which perform four different arithmetical operation on number X and Y.
- 12 Design an Arithmetic unit which performs any four different arithmetic operations on 4-bit binary numbers A and B.
- 13 Design Arithmetical unit which perform following operations on two bits numbers A and B.
 1. Addition of A and B. $(A+B)$
 2. Addition of A and B with carry. $(A+B+1)$
 3. Subtraction of A and B using 1's complement method. $(A+B')$
 4. Subtraction of A and B using 2's complement method. $(A+B'+1)$
- 14 What is the output (F) of following circuit?



 - 15 Determine the value of output F for the following circuit.



- 16 Draw a single block of logical unit which can perform following operation of A1 and B1.
 - (i) A1 and B1
 - (ii) A1 xor B1
 - (iii) A1 or B1
 - (iv) not(A1)

- 17 Design an arithmetic circuit with a selection variables S , that generates the following arithmetic operations. Draw the logic diagram of one typical stage.

S	$C_{in}=0$	$C_{in}=1$
0	$F=A+B$	$F=A+B+1$
1	$F=A-1$	$F=A$

- 18 Draw a logical diagram using parallel adder block for the following Operations:
1. Addition of A and B with carry
 2. Subtraction of A and B using 2's complement method.
- 19 Design a logical unit which can perform four different logical operations of A and B n -bit binary data.
- 20 Design an arithmetic circuit with two selection variables, S_1 and S_0 , that generates the following arithmetic operations. Draw the logic diagram of one typical stage.

S_1	S_0	$C_{in}=0$	$C_{in}=1$
0	0	$F=A$	$F=A+1$
0	1	$F=A+B$	$F=A+B+1$
1	0	$F=A-1$	$F=A$
1	1	$F=A+B'$	$F=A+B'+1$

- 21 Design logical unit which perform following eight logical operation on number A and B .
1. $A \text{ XOR } B$
 2. $A \text{ XNOR } B$
 3. $A \text{ AND } B$
 4. $A \text{ OR } B$
 5. $A \text{ NAND } B$
 6. $A \text{ NOR } B$
 7. Complement of A
 8. Transfer of A
- 22 Draw a logical diagram using parallel adder block for the following operations.
1. Subtraction of A and B using 1's complement method
 2. Subtraction of A and B using 2's complement method
- 23 Explain the Zero flag(bit) in status register with proper logical diagram.
- 24 Draw one stage of logical unit which performs following Logical operations.
 $A_i + B_i$, $(A_i \text{ XOR } B_i)$
- 25 Draw a logical diagram using parallel adder block for the following operations a.
1. Decrement of A .
 2. Transfer of A
- 26 Design logical unit which perform (a) AND (b) OR (c) Ex-OR (d) NOT operation of number A and B .
- 27 Design Arithmetical unit which perform following operations on two numbers A and B of two bits. The operations are:
1. Transfer of A
 2. Increment A by 1
 3. Addition of A and B .
 4. Addition of A and B with carry.